

4-1 Register Transfer Language

- ◆ **Microoperation**: 레지스터에 저장되어있는 데이터 간 연산을 하는 것

The operations executed on data stored in registers (*shift, clear, load, count*)

- ◆ **Internal H/W Organization** (*best defined by specifying*)

1. The set of registers (register의 개수, 종류, 기능)
2. The sequence of microoperations
3. The sequence control of microoperations

칩
CPU마다 다르다

4-2 Register Transfer

- ◆ **Registers**: **Fig. 4-1** 종류

Designated by Capital Letter (*sometimes followed by numerals*): MAR (Memory Address Register), PC (Program Counter), IR (Instruction Register), R1 (Processor Register)

프로그램의 명령어에서 : 다음에 수행될
현재 수행의 다음에 : 명령어의 주소를
수행될 명령어를 저장 : MAR로 부터 받아
명령어 수행

주소저장


4-2. Register Transfer

2/18

The individual F/Fs in an n-bit register : numbered in sequence from 0(*rightmost position*) through n-1

The numbering of bits in a 16-bit register : marked on top of the box

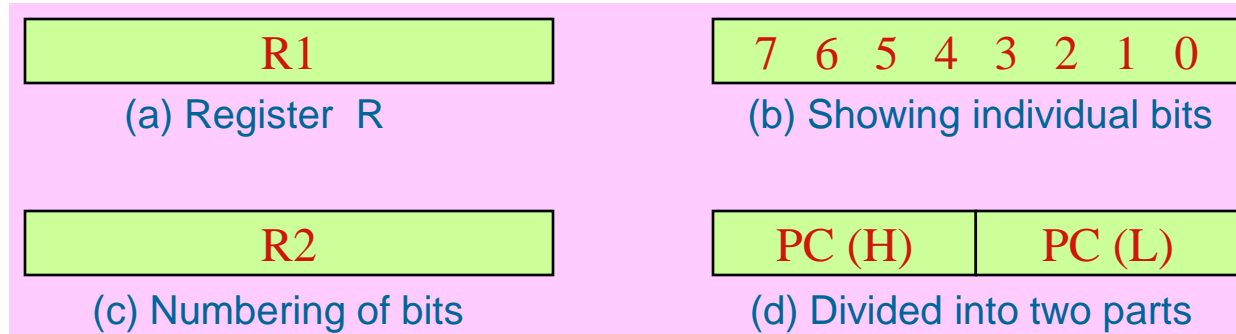A 16-bit register partitioned into two parts : bit 0-7(*symbol “L” Low byte*), bit 8-15(*symbol “H” High byte*)



레지스터 나누기 가능

Figure 4-1. Block diagram of register

여러 형태로 레지스터 표시 가능

4-3 Bus and Memory Transfers

◆ Common Bus : 데이터가 이동하는 통로

A more efficient scheme for transferring information between registers in a **multiple-register configuration**

A bus structure = a set of common lines **비트당 버스 1개 필요**

Control signals determine which register is selected

- » One way of constructing a common bus system is with **multiplexers**
- » The **multiplexers** select the source register whose binary information is place on the bus


The construction of a bus system for four registers : Fig. 4-3

- » 4 bit register X 4
- » Four 4 X 1 Multiplexers
- » Bus Selection : S0, S1

S1	S0	Register selected
0	0	A
0	1	B
1	0	C
1	1	D

8 Registers with 16 bit

- » 16 X 1 mux 8 개 필요

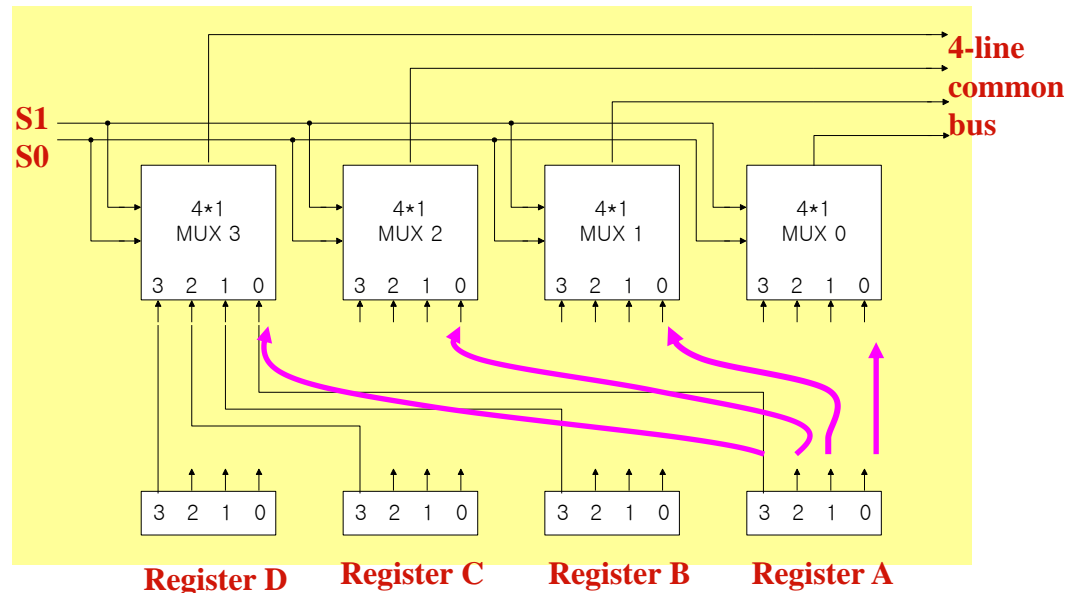

4-4. Arithmetic Microoperation

4 / 18

◆ 4-bit Binary Adder : Fig. 4-6

추가산기 Full adder = 2-bits sum + previous carry

Binary adder = the arithmetic sum of two binary numbers of any length

c_0 (input carry), c_4 (output carry)

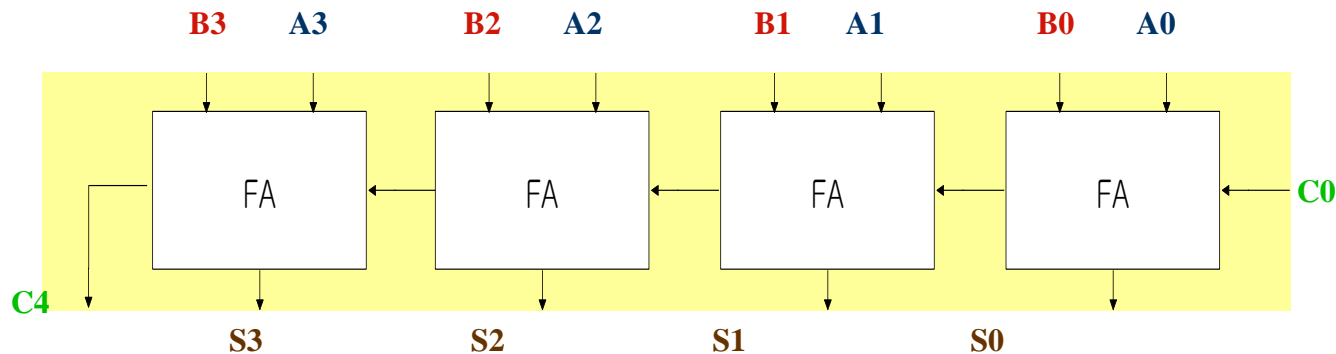


Figure 4-6. 4-bit binary adder

FA가 4개

4-4. Arithmetic Microoperation


5/18

◆ 4-bit Binary Adder-Subtractor : *Fig. 4-7* ^{회로} 덧셈기로 ^{회로} 뺄셈이 구현 가능

One common circuit by including an exclusive-OR gate with each full-adder

$M=0$: Adder $B \oplus M + C = B \oplus 0 + 0 = B$, $\therefore A + B$

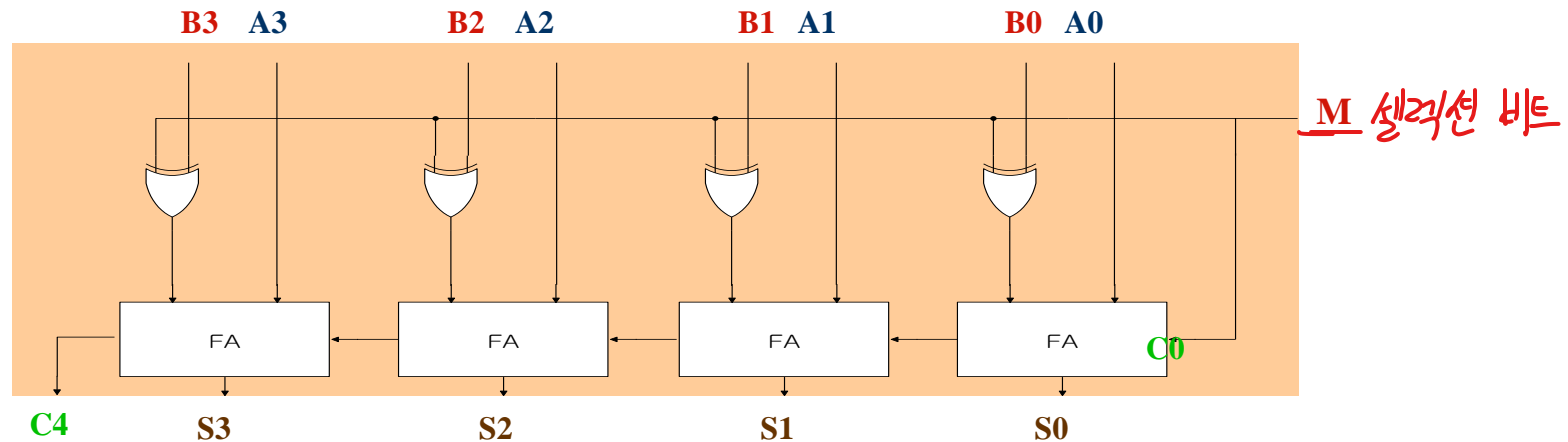$M=1$: Subtractor $B \oplus M + C = B \oplus 1 + 1 = B' + 1 = -B(2's \text{ comp})$, $\therefore A - B$



4-4. Arithmetic Microoperation

6/18

◆ Arithmetic Circuit

One composite arithmetic circuit in **Tab. 4-4** :

Fig. 4-9

$$D = A_0(X_0) + B_0(Y_0) + C_{in}$$

» B_0 : S_0, S_1 에 따라 **$B, \bar{B}, 0, 1$**

» Tab. 4-4의 Input $Y = B$


선택지 예시

Select			Input	Output	Microoperation
S_1	S_0	C_{in}	Y	$D = A + Y + C_{in}$	
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

$$A + 1111 = A - 1$$

$$A - 1 + 1 = A$$

$$A + B' = A + B' + 1 - 1 = A - B - 1$$

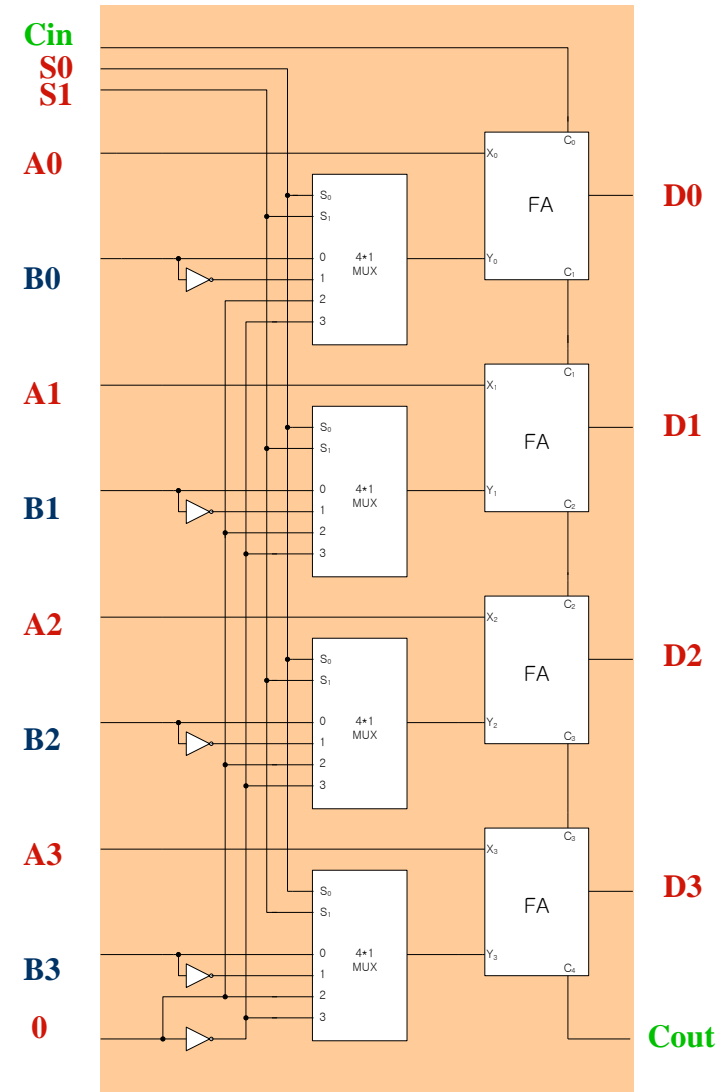

4-5. Logic Microoperation

7/18

레지스터에 저장되어있는 데이터를 대상으로 논리 연산

4-5 Logic Microoperation

◆ Logic microoperation

Logic microoperations consider **each bit of the register separately** and treat them as binary variables

» exam)

$$P: R1 \leftarrow R1 \oplus R2$$

$$\begin{array}{r} 1010 \text{ Content of R1} \\ + 1100 \text{ Content of R2} \\ \hline 0110 \text{ Content of R1 after P=1} \end{array}$$

Special Symbols

» Special symbols will be adopted for the logic microoperations **OR(\vee)**, **AND(\wedge)**, and **complement(a bar on top)**, to distinguish them from the corresponding symbols used to express Boolean functions

» exam)

$$P + Q: R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$$

Logic OR

Arithmetic ADD

Arithmetic에서
1's Complement
와 동일

◆ List of Logic Microoperation

Truth Table for 16 functions for 2 variables : **Tab. 4-5 (뒷면에...)**


16 Logic Microoperation : **Tab. 4-6**

◆ Hardware Implementation

16 microoperation → Use only 4(AND, OR, XOR, Complement)

One stage of logic circuit : **Fig. 4-10**

∴ All other Operation
can be derived

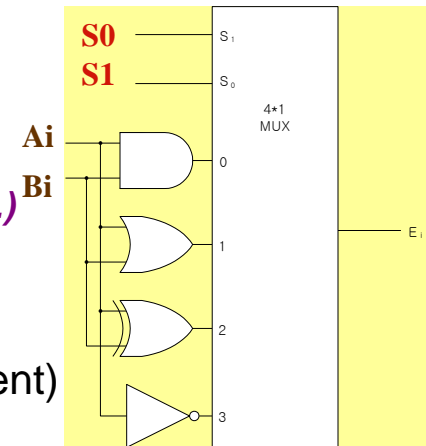

4-5. Logic Microoperation

8/18

4비트의 디코더는 16개 중 1개를 택할 수 있는 예시

X	Y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

TABLE 4-5. Truth Table for 16 Functions of Two Variables

식을 외우지 말고, 식을 보고 구현할 줄 알기

Boolean function	Microoperation	Name	Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear	$F_8 = (x+y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_1 = xy$	$F \leftarrow A \wedge B$	AND	$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Ex-NOR
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$		$F_{10} = y'$	$F \leftarrow \overline{B}$	Compl-B
$F_3 = x$	$F \leftarrow A$	Transfer A	$F_{11} = x+y'$	$F \leftarrow A \vee \overline{B}$	
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$		$F_{12} = x'$	$F \leftarrow \overline{A}$	Compl-A
$F_5 = y$	$F \leftarrow B$	Transfer B	$F_{13} = x'+y$	$F \leftarrow \overline{A} \vee B$	
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Ex-OR	$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_7 = x+y$	$F \leftarrow A \vee B$	OR	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	set to all 1's

TABLE 4-6. Sixteen Logic Microoperations

&& : 일반적 AND 연산자
& : 비트 연산자 (0, 1)

4-5. Logic Microoperation

9/18

◆ Some Applications

Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register

Used to change bit values, delete a group of bits, or insert new bit values

Selective-set $A \leftarrow A \vee B$

- » The selective-set operation sets to 1 the bits in register A where there are corresponding 1's in register B. It does not effect bit positions that have 0's in B

Selective-complement $A \leftarrow A \oplus B$

- » The selective-complement operation complements bits in A where there are corresponding 1's in B. It does not effect bit positions that have 0's in B

1 → 0

Selective-clear $A \leftarrow A \wedge \bar{B}$

- » The selective-clear operation clears to 0 the bits in A only where there are corresponding 1's in B

0 → 0

Selective-mask $A \leftarrow A \wedge B$

- » The mask operation is similar to the selective-clear operation except that the bits of A are cleared only where there are corresponding 0's in B

여러 비트 중에서, 선택된 비트에 대해서만 비트 논리 연산을 수행해라

1010 A before

1100 B(Logic Operand)

1110 A After

Selective-set

1010 A before

1100 B(Logic Operand)

0110 A After

Selective-complement

1010 A before

1100 B(Logic Operand)

0010 A After

Selective-clear

1010 A before

1100 B(Logic Operand)

1000 A After

Selective-mask

Insert

- » The insert operation inserts a new value into a group of bits
- » This is done by first masking the bits and then ORing them with the required value

1) Mask		2) OR		Clear
0110 1010 A before		0000 1010 A before		1010 A
0000 1111 B mask	→	1001 0000 B insert		1010 B
0000 1010 A after mask		1001 1010 A after insert		0000 A after clear

Clear $A \leftarrow A \oplus B$

- » The clear operation compares the words in A and B and produces an all 0's result if the two numbers are equal

4-6 Shift Microoperations

◆ Shift Microoperations : Tab. 4-7


Shift microoperations are used for serial transfer of data

Three types of shift microoperation : **Logical**, **Circular**, and **Arithmetic**

◆ Logical Shift

- { = A **logical shift** transfers 0 through the serial input
- The bit transferred to the end position through the serial input is assumed to be 0 during a logical shift (**Zero inserted**)

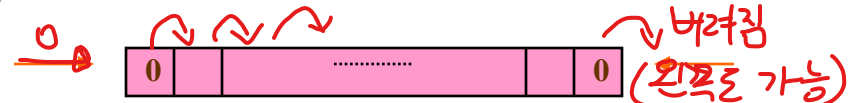$R1 \leftarrow shl R1$
 $R2 \leftarrow shr R2$



4-6. Shift Microoperation 3종류 있다 11/18

logical


Symbolic designation	Description
1 $R \leftarrow \text{shl } R$ 왼	Shift-left register R
$R \leftarrow \text{shr } R$ 오	Shift-right register R
2 $R \leftarrow \text{cil } R$ 왼	Circular shift-left register R
$R \leftarrow \text{cir } R$ 오	Circular shift-right register R
3 $R \leftarrow \text{ashl } R$ 왼	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$ 오	Arithmetic shift-right R

TABLE 4-7. Shift Microoperations

◆ Circular Shift(Rotate)

The **circular shift** circulates the bits of the register around the two ends without loss of information

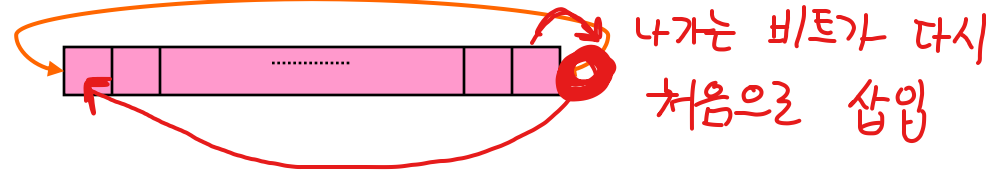$R1 \leftarrow cil\ R1$
 $R2 \leftarrow cir\ R2$



◆ Arithmetic Shift

An **arithmetic shift** shifts a **signed** binary number to the left or right

An arithmetic **shift-left multiplies** a signed binary number by 2

An arithmetic **shift-right divides** the number by 2

Arithmetic shifts must leave the sign bit unchanged because the sign of the number remains the same

$\div 2$ Shift right : $R2 \leftarrow ashr\ R2$

Sign bit unchanged



MSB LSB
 부호비트를 고려해 부호바뀔 위험X

Sign reversal occur : Overflow F/F $V_s=1$

$$V_s = R_{n-1} \oplus R_{n-2}$$

$\times 2$ Shift left : $R2 \leftarrow ashl\ R2$

LSB lost

Carry out Sign bit



0 insert

R_{n-1} R_{n-2} ... R_1 R_0
 MSB LSB



Overflow F/F로 전송

$V_s=1$: Overflow


$V_s=0$: 정상

부호비트 변화X

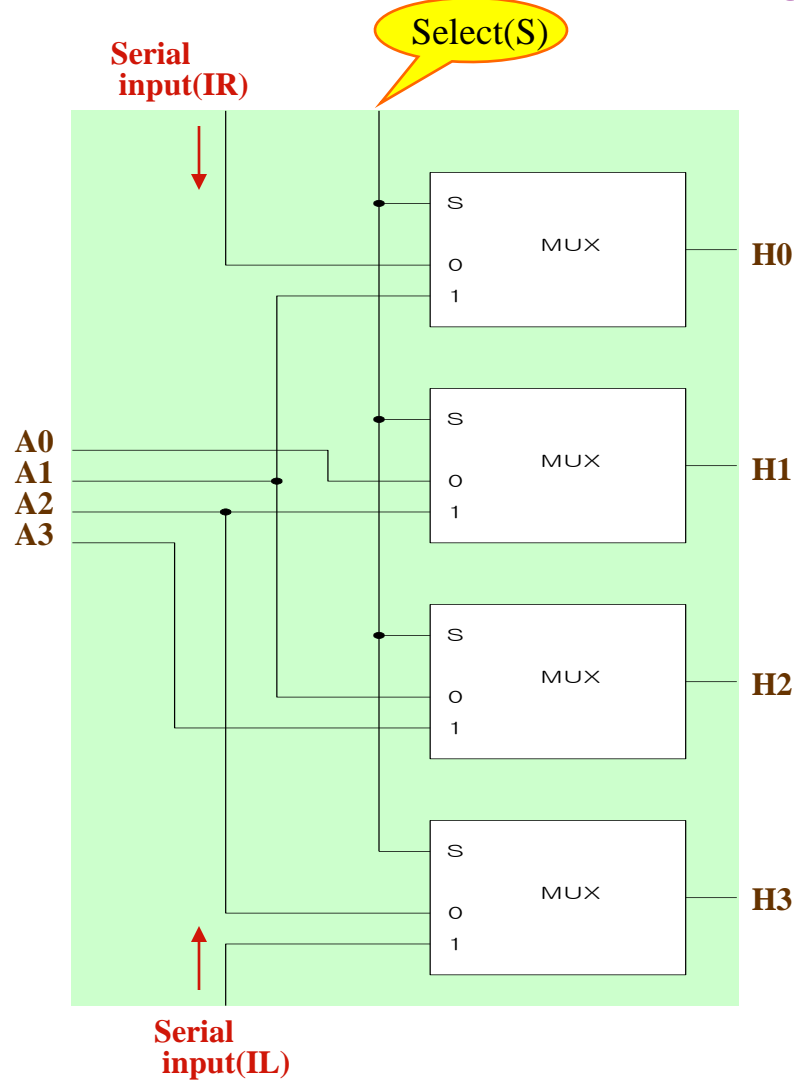4-7. Arithmetic Logic Shift Unit ^{한개씩}

13/18

◆ Hardware Implementation(Shifter) : Fig. 4-12



Function Table				
Select	output			
S	H0	H1	H2	H3
0	IR	A0	A1	A2
1	A1	A2	A3	IL

4 -7. Arithmetic Logic Shift Unit

14 / 18

4-7 Arithmetic Logic Shift Unit

◆ One stage of arithmetic logic shift unit : **Fig. 4-13**

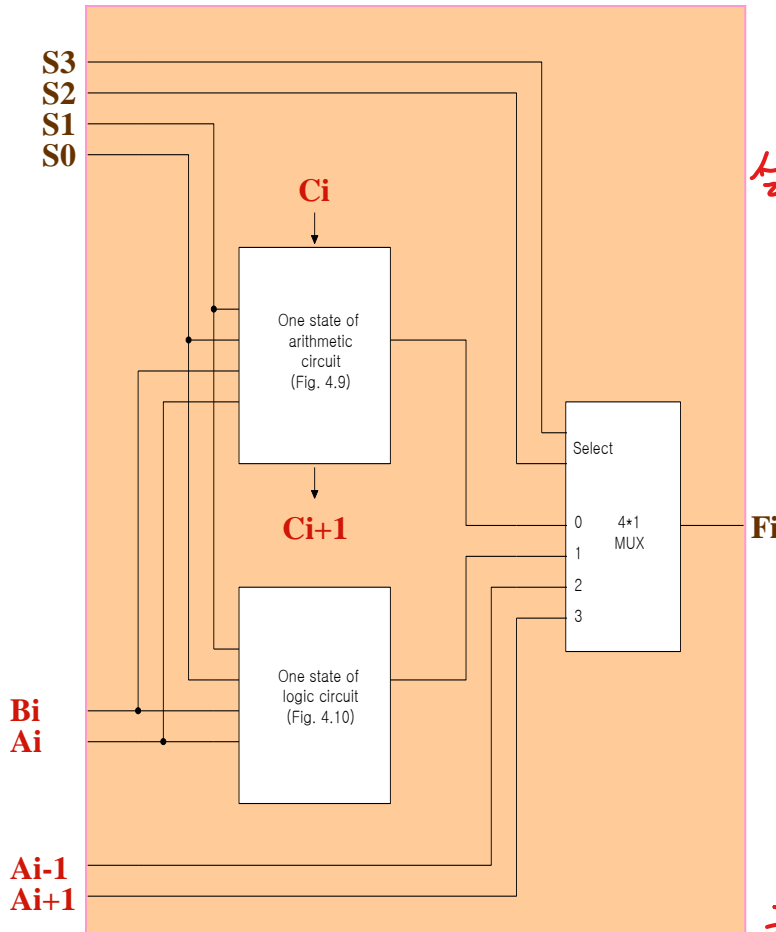


Table 4-8. Function Table for Arithmetic Logic Shift Unit

Operation select					Operation	Function
<i>신규</i> S ₃	S ₂	S ₁	S ₀	<i>기존</i> C _{in}		
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B$	Subtract with borrow
0	0	1	0	1	$F = A + B + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	×	$F = A \wedge B$	AND
0	1	0	1	×	$F = A \vee B$	OR
0	1	1	0	×	$F = A \oplus B$	XOR
0	1	1	1	×	$F = A$	Complement A
1	0	×	×	×	$F = \text{shr } A$	Shift right A into F
1	1	×	×	×	$F = \text{shl } A$	Shift left A into F

즉, 여러 종류의 Microoperation 이 혼재가능